

## g47\_7\_segment\_decoder

7-segment Decoder circuit

### Description:

The 7-segment Decoder circuit takes as input a 5-bit encoded value (CODE) which drives a 7-bit 7-segment display (SEGMENTS). The code represents a letter from A (0) to Z (25) which turns on segments that are active-low (turned on when driven low).

### Input:

CODE (5-bits) - encoded value

### Output:

SEGMENTS (7-bits) - segments necessary to represent the letter

### Diagram:

### Testing: