ECSE 323 — Group 47 Lab 4 Report Permutation

Junyoung Shin id. 260499663 Timothee Flichy id. 260557686

April 1, 2016

1 Permutation

The permutation is used encript and revert to the original message. To do so, we were given a table which depics the character encription list given in the figure 1. There are 4 configuration we are given to be made. To make the permutation circuit, we need 2 input and 2 outputs. The inputs will receive a 2 bit rotor_type giving which type of encription that must be done and the second input inputs a 5 bit input_code that must be encripted. The outputs are a 5 bit output_code which outputs the encripted version of the input bits determined by the rotery position and the second input is the inv_output_code giving out the inverted or decripted 5 bit code. This is given by the figure 2. We tested out vhdl code on the ModelSim and got what we were expected to get from the permutation graph

INPUT	Α	В	С	D	E	F	G	Н	Ι	J	K	L	\mathbf{M}	N	o	P	Q	R	S	T	U	V	W	Х	Y	Z
Rotor I	Ε	K	М	F	L	G	D	Q	V	Z	И	Т	0	W	Y	Η	Х	U	S	P	Α	Ι	В	R	С	J
Rotor II	Α	J	D	K	S	Ι	R	U	X	В	L	Н	W	Т	M	С	Q	G	Z	И	Ρ	Y	F	V	0	Ε
Rotor III	В	D	F	Η	J	L	С	Ρ	R	Т	Х	V	Z	И	Y	Ε	Ι	W	G	A	K	M	U	S	Q	0
Rotor IV	Ε	S	0	V	Ρ	Z	J	A	Y	Q	U	Ι	R	Η	Х	L	И	F	Т	G	K	D	С	M	W	В

Figure 1: Permutation graph.

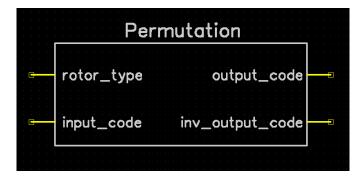


Figure 2: Permutation symbol.

as you can see from the figures 3, 4, 5, 6, and 7.



Figure 3: Tested circuit on ModelSim



Figure 4: With rotor I.



Figure 5: With rotor II.



Figure 6: With rotor III.



Figure 7: With rotor V.