

Group 47  
Timothee Flichy - 260557686  
Jun Young Shin - 260499663

## g47\_5\_26\_Decoder

### Description:

Our decoder circuit takes a 5-bit binary number input (INDEX), representing a number from 0 to 31, and decodes it to assert one of 26 output lines (D). The circuit produces an error signal if the input is greater than 25 (ERROR).

### Input:

INDEX signal (5 bits) - binary number to be decoded

### Output:

D signal (26 bits) - separate (decoded) output lines


ERROR signal (1 bit) - Error signal (for numbers outside of range)

### Diagram:

### Schematic:
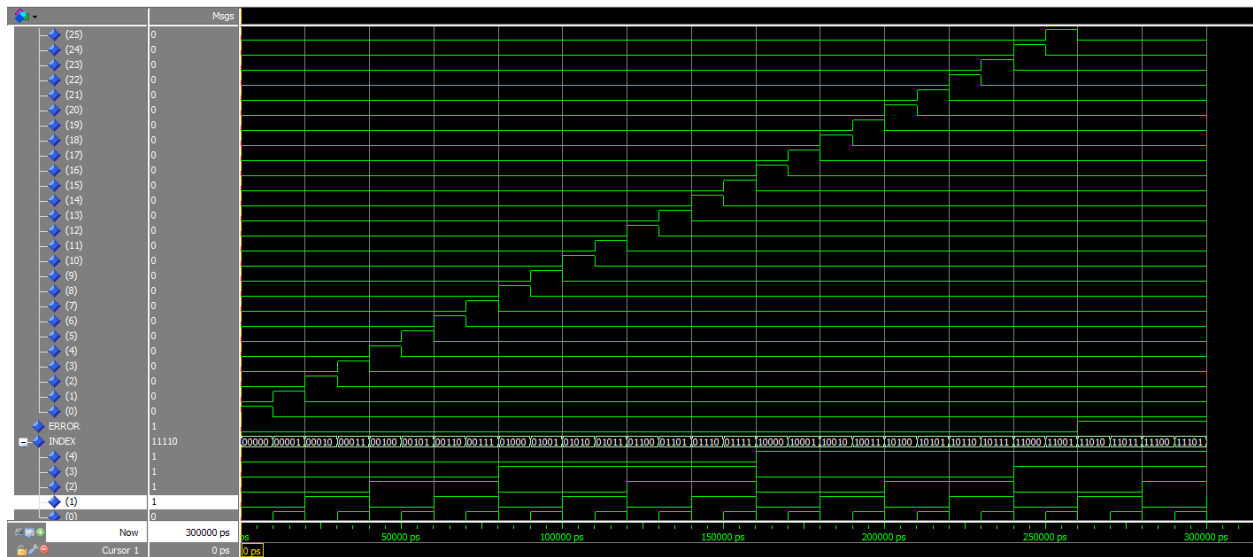
### Testing:

In order to test our circuit, we used exhaustive testing by observing the output of every valid input. We know the circuit works correctly because, according to the image below, every input provides the desired output.



### A - Boolean Equations:

$$e = AB \cdot (C + D)$$

$$P_{16} = A\bar{B}\bar{C}\bar{D}\bar{E}$$

$$D_{11} = A B C \bar{D} E$$

$$D_{14} = A B C D E$$

$$D_{19} = A \text{ } \cancel{B} \text{ } CDE$$

$$D_{26} = A \bar{B} C \bar{D} \bar{E}$$

$$D_{21} = A \bar{B} C \bar{D} E$$

$$D_{21} = A \bar{B} C D E$$

$$D_{23} = A\bar{B}CDEF$$

$$D_{24} = AB\bar{C}\bar{D}\bar{E}$$

$$D_{25} = A \bar{B} \bar{C} \bar{D} E$$